

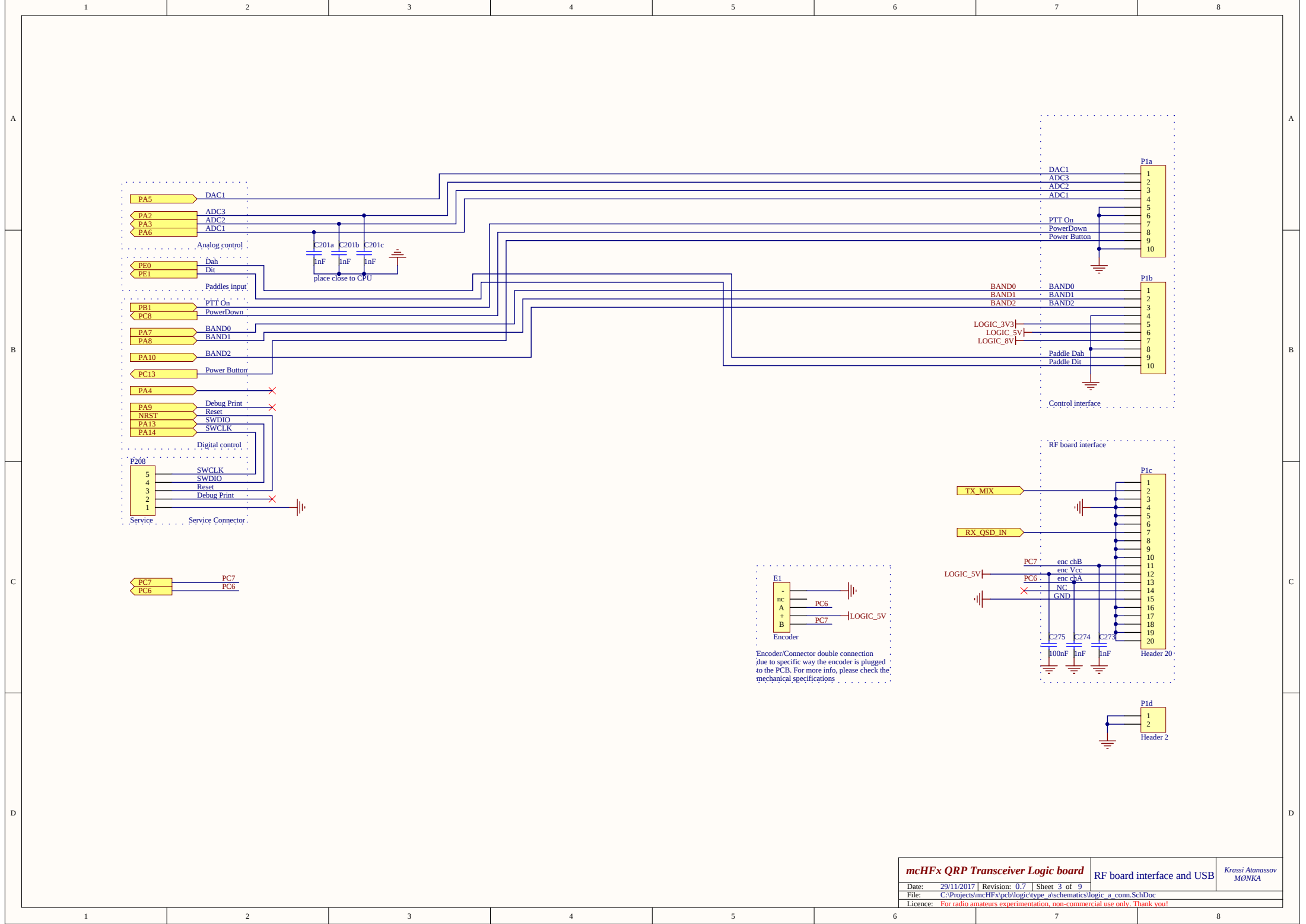


 

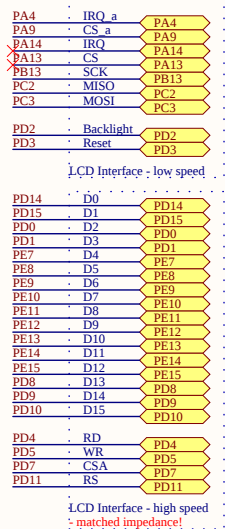

A

B

C


D

A

B


C

D

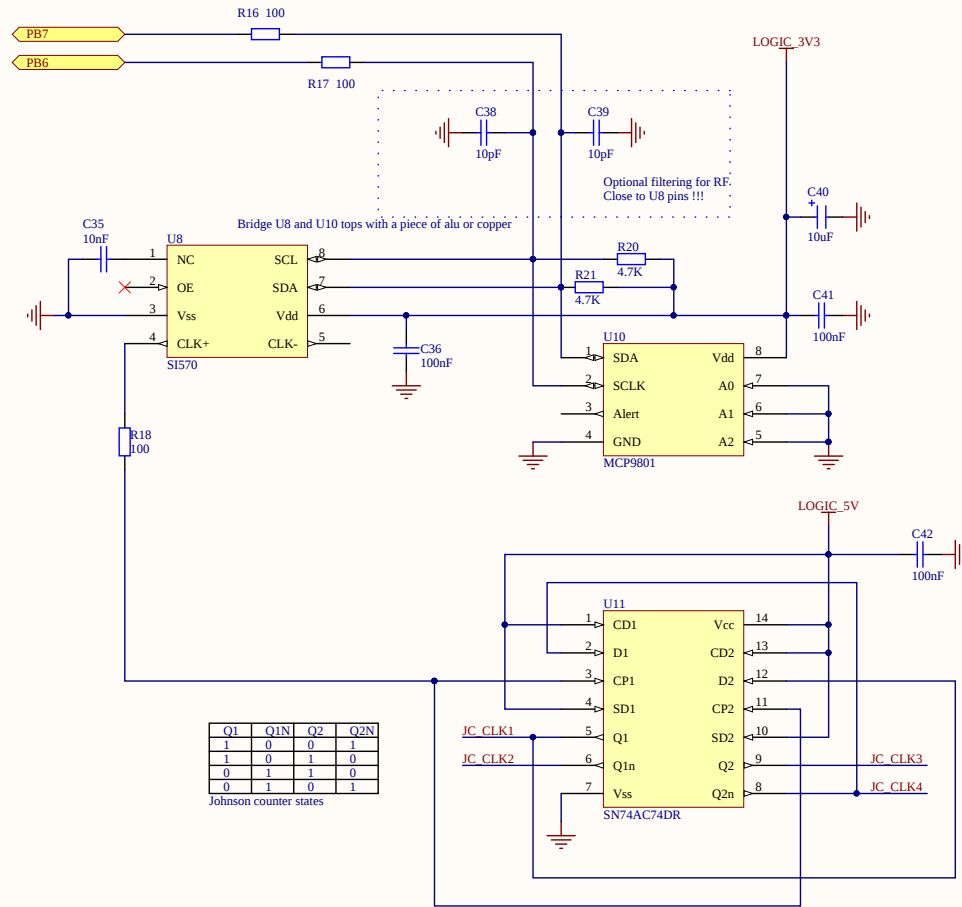


Q1	Q1N	Q2	Q2N
1	0	0	1
1	0	1	0
0	1	1	0
0	1	0	1


Johnson counter states

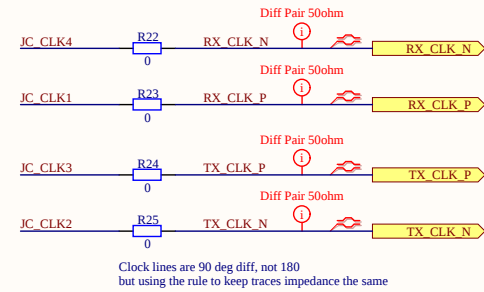


S1	S0	S1	S0
1	1	0	0
1	0	0	1
0	0	1	1
0	1	1	0


RX clock TX clock

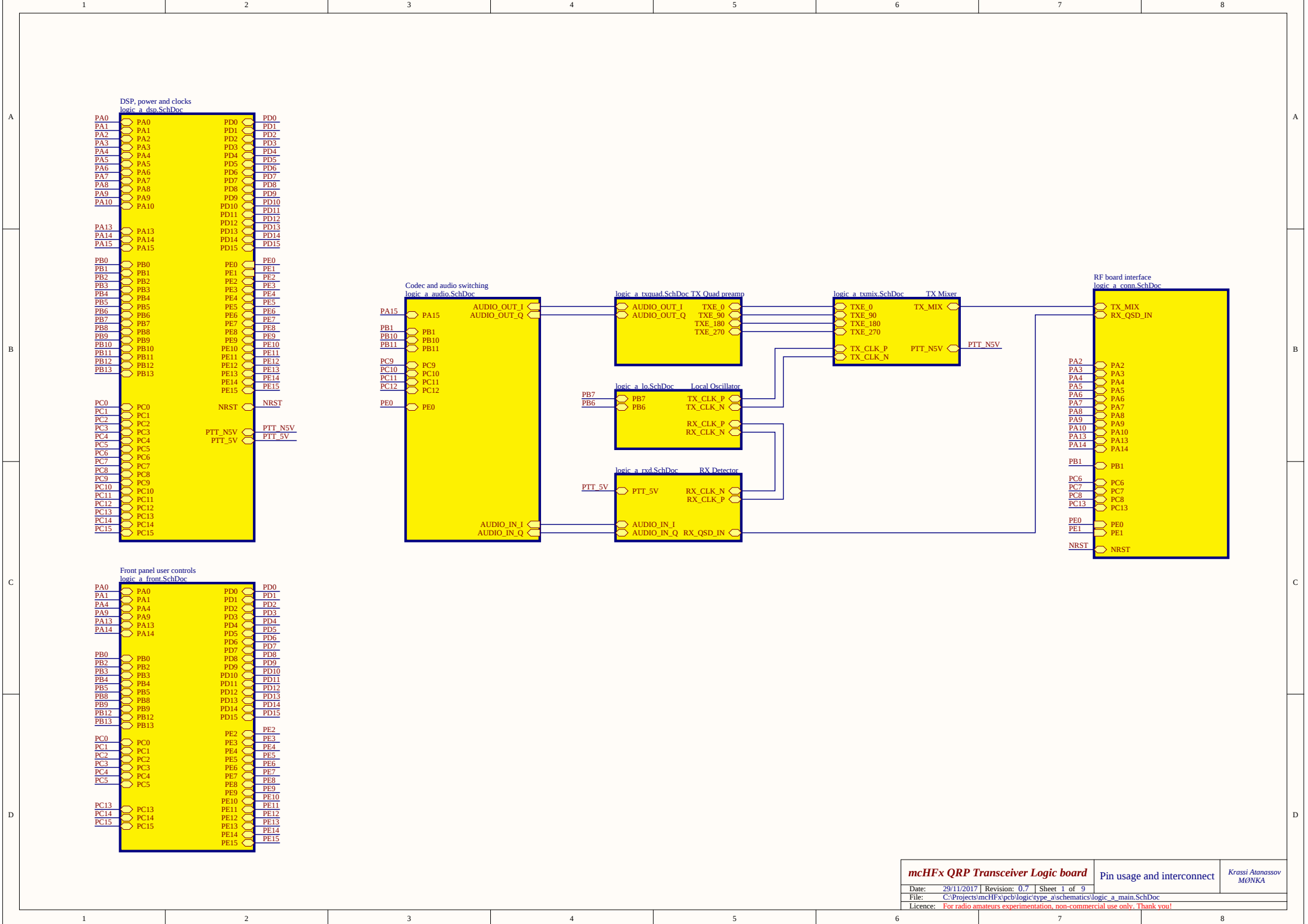

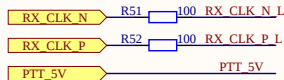

MODE	OE	S1	S0	Switches	Phases
RX	0	0	0	1B1	270
RX	0	0	1	2B2	0
RX	0	1	1	1B4	90
RX	0	1	0	2B3	180
TX	1	X	X	All Open	

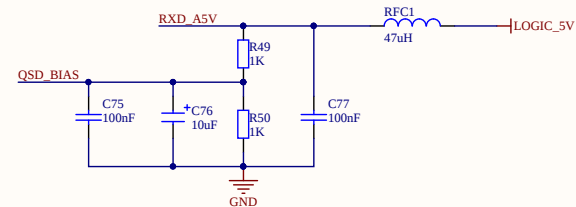

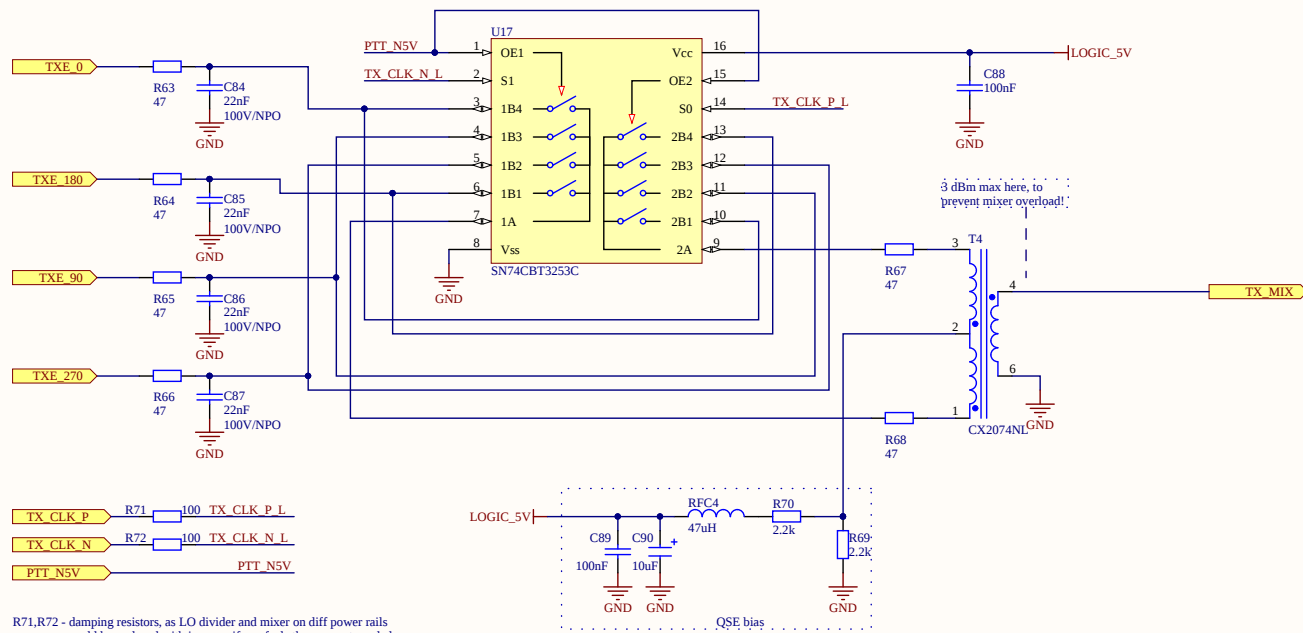

R71,R72 - damping resistors, as LO divider and mixer on diff power rails could be replaced with jumpers if one feels they are not needed

MODE	OE	S1	S0	Switches	Phases
TX	0	0	0	1B1/2B1	180/0
TX	0	0	1	2B2/1B2	90/270
TX	0	1	1	1B4/2B4	0/180
TX	0	1	0	2B3/1B3	270/90
RX	1	X	X	All Open	

